

5th Homework - Solution

- In this homework, we shall exercise the modeling of a simple electrical circuit using bond graphs.
- We shall also model the same electrical circuit using a circuit diagram (a wrapped bond graph).
- We shall finally determine the overhead associated with the wrapping technique.

October 25, 2012


© Prof. Dr. François E. Cellier

Start Presentation



Electrical Circuit

- Given the following circuit:

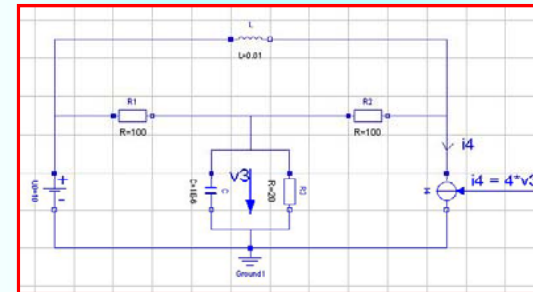

October 25, 2012

© Prof. Dr. François E. Cellier

Start Presentation



Electrical Circuit II

- The circuit is to be modeled using bond graphs without wrapping.
- Use a sensor (detector) element together with a modulated source element to implement the non-linear current source in the circuit.
- Simulate the circuit during 50 μsec , and plot v_3 as a function of time.


October 25, 2012

© Prof. Dr. François E. Cellier

Start Presentation



Bond Graph of Circuit

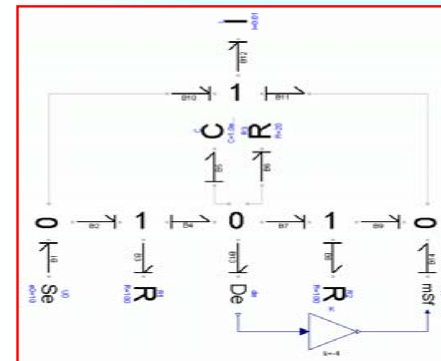


- Since flow sources in bond-graphic notation are defined with their positive flow pointing *into* the system, we need to make the gain factor negative in order to compensate for the directional sign change.

October 25, 2012

© Prof. Dr. François E. Cellier

Start Presentation





Eidgenössische Technische Hochschule Zürich

Swiss Federal Institute of Technology Zürich

Mathematical Modeling of Physical Systems

Simulation Results

Variables

Values

Size

uIn[1]

uOut[1]

uIn[2]

uOut[2]

uIn[3]

uOut[3]

uIn[99]

uOut[99]

Plot (1.1)

0.05

0.04

0.03

0.02

0.01

0.00

-0.01

0.00

1.5e-5

3.0e-5


4.5e-5

6.0e-5

October 25, 2012

© Prof. Dr. François E. Cellier

Start Presentation



Eidgenössische Technische Hochschule Zürich

Swiss Federal Institute of Technology Zürich

Mathematical Modeling of Physical Systems


Electrical Circuit III

- The circuit is to be modeled using bond graphs with wrapping, i.e., using the bond graph electrical library.
- Simulate the circuit during $50 \mu\text{sec}$, and plot v_3 as a function of time.
- Compare the number of initial and final equations as well as the simulation time with those obtained in the unwrapped bond-graph solution.

October 25, 2012

© Prof. Dr. François E. Cellier

Start Presentation




Eidgenössische Technische Hochschule Zürich

Swiss Federal Institute of Technology Zürich

Mathematical Modeling of Physical Systems


Bond Graph Electrical Library Model

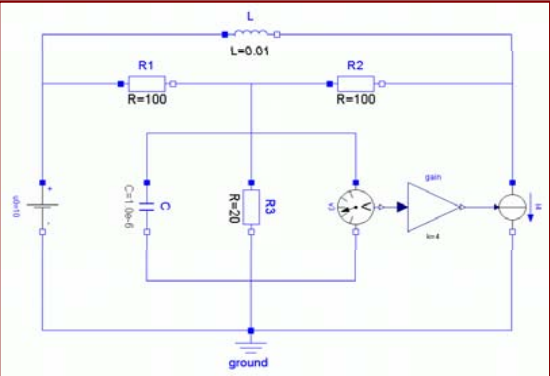

October 25, 2012

© Prof. Dr. François E. Cellier

Start Presentation



Eidgenössische Technische Hochschule Zürich

Swiss Federal Institute of Technology Zürich

Mathematical Modeling of Physical Systems

Comparison of Translation Logs

Syntax Error

Translation

Dialog Error

Simulation

Translation of `translatabl_5.bgl`

DrE having 228 scalar unknowns and 228 scalar equations

STATISTICS

Original Model

Number of components: 30

Variables: 208

Constants: 2 (17 scalars)

Parameters: 201 (222 scalars)

Unknowns: 201 (222 scalars)

Overdetermined variables: 2 scalars

Equations: 185

Nominal: 185

Translated Model

Constants: 52 scalars

Free parameters: 7 scalars

Parameter dependent: 2 scalars

Inputs: 0

Outputs: 0

Continuous time states: 2 scalars

Time-varying variables: 12 scalars

Algebraic variables: 194 scalars

Assumed default initial conditions: 2

LogRefInitialConditions: gives more information

Number of mixed real-discrete systems of equations: 0

Sizes of linear systems of equations: 13

Sizes after manipulation of the linear systems: 13

Sizes of nonlinear systems of equations: 13

Sizes after manipulation of the nonlinear systems: 13

Number of numerical Jacobians: 0

Finished

27 equations StopTime=5e-005

Finished

Syntax Error

Translation

Dialog Error

Simulation

Translation of `translatabl_5.bgl`

DrE having 441 scalar unknowns and 441 scalar equations

STATISTICS

Original Model

Number of components: 67

Variables: 425

Constants: 0

Parameters: 17 (17 scalars)

Unknowns: 408 (441 scalars)

Overdetermined variables: 4 scalars

Equations: 317

Nominal: 147

Translated Model

Constants: 190 scalars

Free parameters: 5 scalars

Parameter dependent: 12 scalars

Inputs: 0

Outputs: 0

Continuous time states: 2 scalars

Time-varying variables: 18 scalars

Algebraic variables: 272 scalars

Assumed default initial conditions: 2

LogRefInitialConditions: gives more information

Number of mixed real-discrete systems of equations: 0

Sizes of linear systems of equations: 13

Sizes after manipulation of the linear systems: 13

Sizes of nonlinear systems of equations: 13

Sizes after manipulation of the nonlinear systems: 13

Number of numerical Jacobians: 0

Finished

27 equations StopTime=5e-005

Finished


October 25, 2012

© Prof. Dr. François E. Cellier

Start Presentation

2

Comparison of Simulation Logs

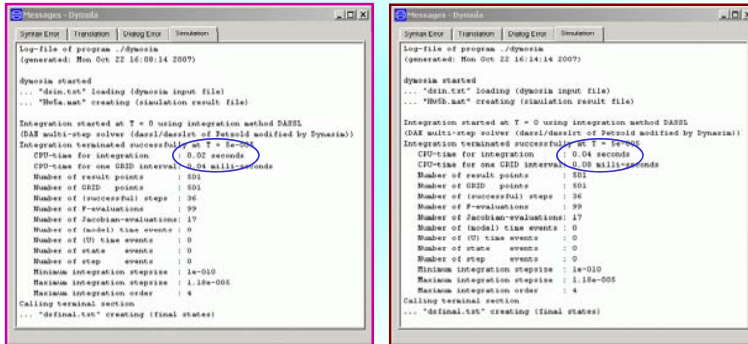

Graphical Model

BG Electrical Model


October 25, 2012

© Prof. Dr. François E. Cellier

Start Presentation



Simulation Results

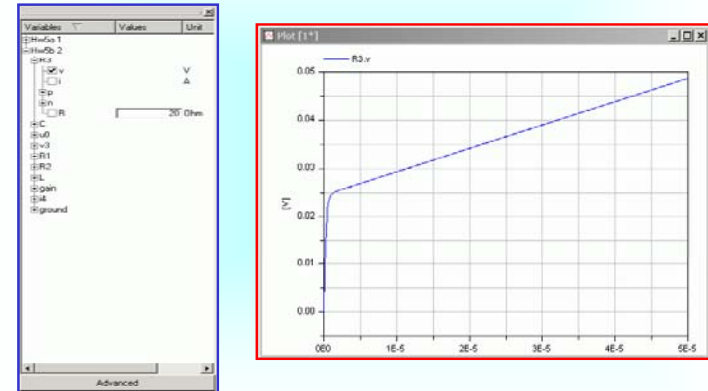

October 25, 2012

© Prof. Dr. François E. Cellier

Start Presentation

