


7th Homework – Solution

- In this homework, we shall model and simulate a discontinuous system as well as train the incorporation of tabular functions.
- We shall first model an electrical oscillatory circuit containing a tunnel diode.
- We shall then model a fly-back electronic power converter circuit with current overprotection.

- Free-running tunnel diode circuit
- Pulsed tunnel diode circuit
- Fly-back electronic power converter circuit

Free-running Tunnel Diode Circuit I

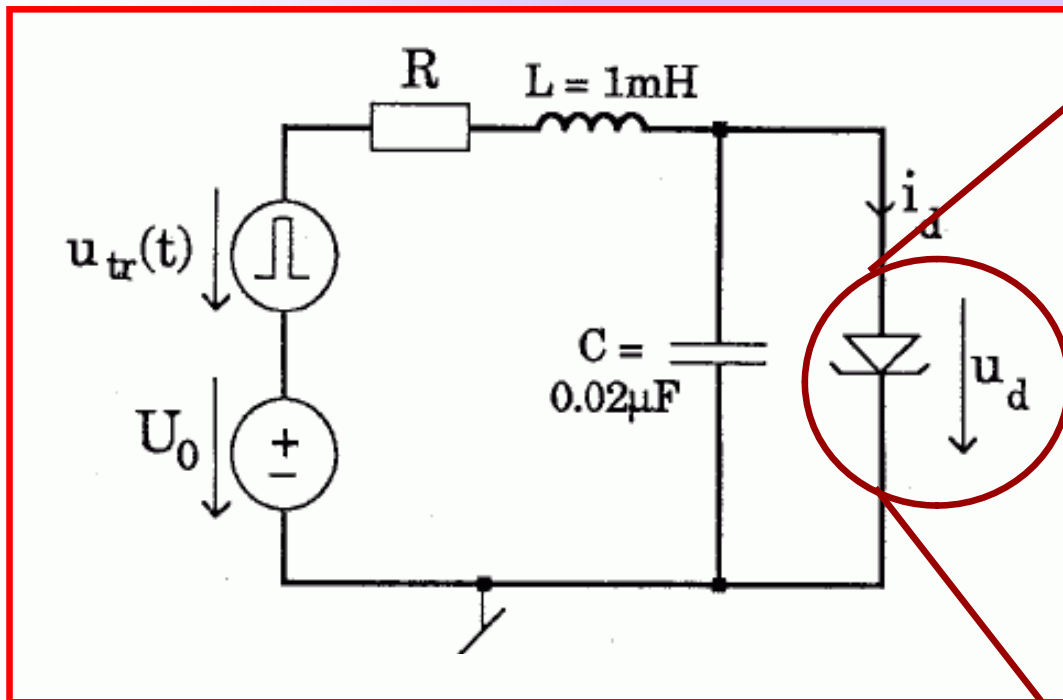
- Given the following electronic circuit:





Voltage u_d [V]	Current i_d [mA]
0.00	0.00
0.05	1.70
0.10	2.90
0.15	4.00
0.20	4.75
0.25	5.00
0.30	4.90
0.35	4.25
0.40	3.20
0.45	2.35
0.50	2.00
0.55	2.20
0.60	2.70
0.65	3.50
0.70	4.35
0.75	5.30
0.90	9.00

Free-running Tunnel Diode Circuit II

- Let us set $U_{tr} = 0$. We select a resistor with a value of $R = 25 \Omega$. We choose a DC bias of $U_0 = 0.48 V$.
- Create a bond graph (without wrapping) of the circuit. Use causal bonds whenever possible.
- Create a model **T3** representing the tunnel diode. The tabular function is incorporated by dragging the corresponding table-lookup block into the diagram window.
- Use Matlab to save the table onto a binary file, and reference that table from within the parameter window of the table-lookup block. Make sure to assign the correct causality to the table-lookup function. You can determine the correct causality from the bond graph of the overall circuit.

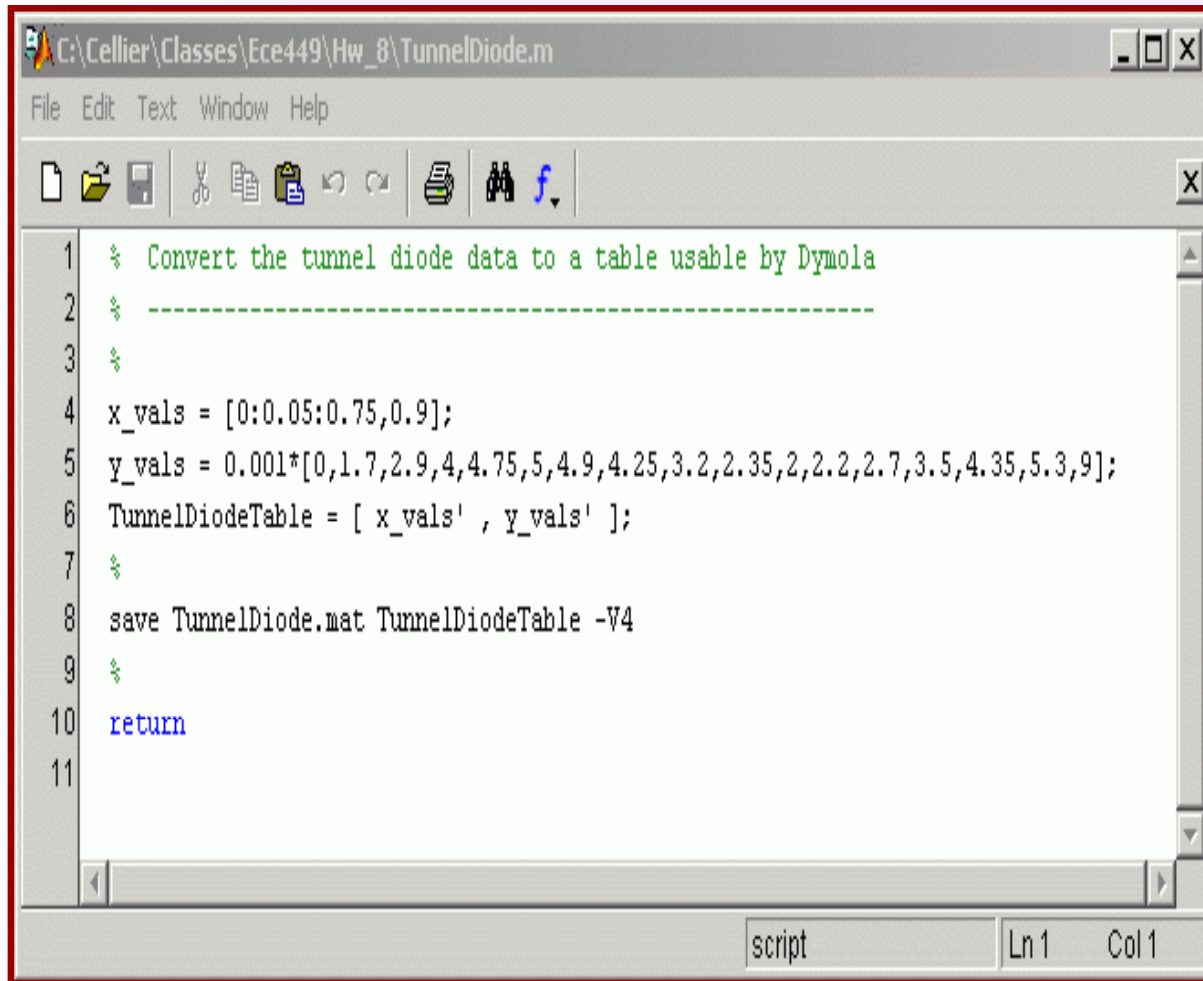
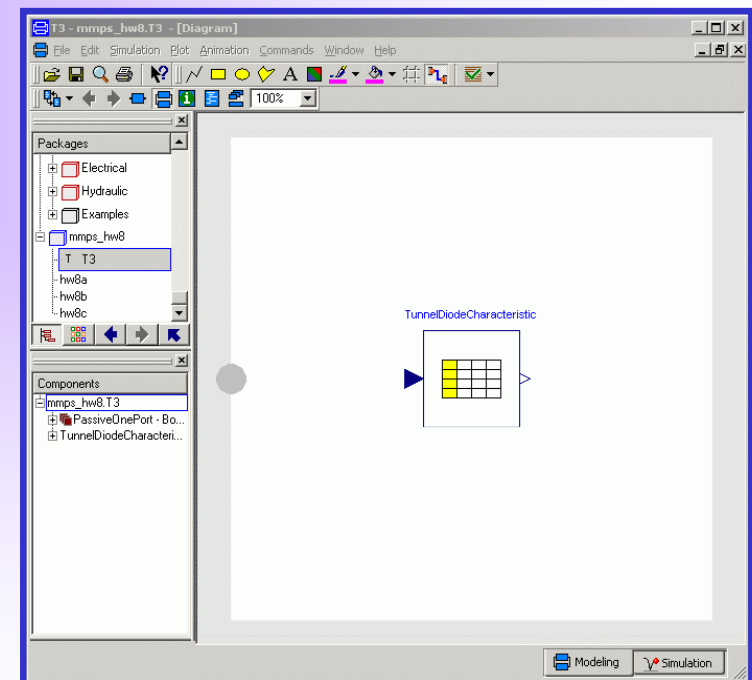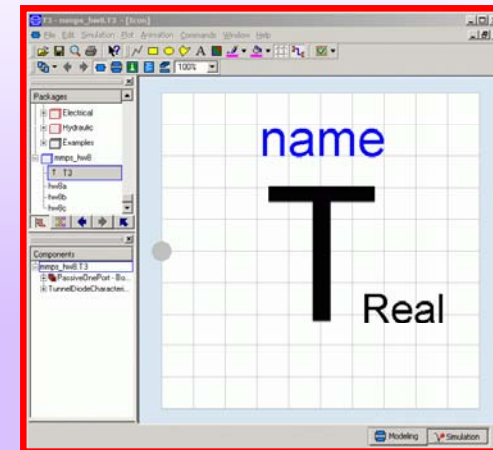
```
1 % Convert the tunnel diode data to a table usable by Dymola
2 % -----
3 %
4 x_vals = [0:0.05:0.75,0.9];
5 y_vals = 0.001*[0,1.7,2.9,4,4.75,5,4.9,4.25,3.2,2.35,2,2.2,2.7,3.5,4.35,5.3,9];
6 TunnelDiodeTable = [ x_vals' , y_vals' ];
7 %
8 save TunnelDiode.mat TunnelDiodeTable -V4
9 %
10 return
11
```



The screenshot displays the Modelica software environment with three main windows:



- Diagram Window (T3 - mmps_hw8.T3 - [Diagram]):** Shows a block diagram with a `TunnelDiodeCharacteristic` block highlighted by a red circle. The block has a yellow and white grid icon.
- Components List:** A tree view on the left showing the project structure: `mmps_hw8` containing `T T3`, `hw8a`, `hw8b`, and `hw8c`. The `TunnelDiodeCharacteristic` block is listed under `mmps_hw8.T3`.
- Modelica Text Editor (T3 - mmps_hw8.T3 - [Modelica Text]):** Contains the following code:


```
model T3 "Real tunnel diode"
  extends BondLib.Interfaces.PassiveOnePort;

  equation
    TunnelDiodeCharacteristic.u = e;
    f = TunnelDiodeCharacteristic.y[1];
end T3;
```
- TunnelDiodeCharacteristic in mmps_hw8.T3 Dialog:** A configuration window for the selected block.
 - General Tab:**
 - Name:** `TunnelDiodeCharacteristic`
 - Comment:** `Tabular data for tunnel diode characteristic`
 - Model Path:** `Modelica.Blocks.Tables.CombiTable1Ds`
 - Comment:** `Table look-up in one dimension (matrix/file) with one input and n outputs`
 - table data definition:**
 - tableOnFile:** `true` (dropdown)
 - fill:** `fill(0.0, 0, 2)` (text field)
 - tableName:** `"TunnelDiodeTable"` (text field)
 - fileName:** `"TunnelDiode.mat"` (text field)
 - data interpretation:**
 - columns:** `2:size(table, 2)` (text field)
 - smoothness:** `Blocks.Types.Smoothness.LinearSegments` (dropdown)


Free-running Tunnel Diode Circuit III

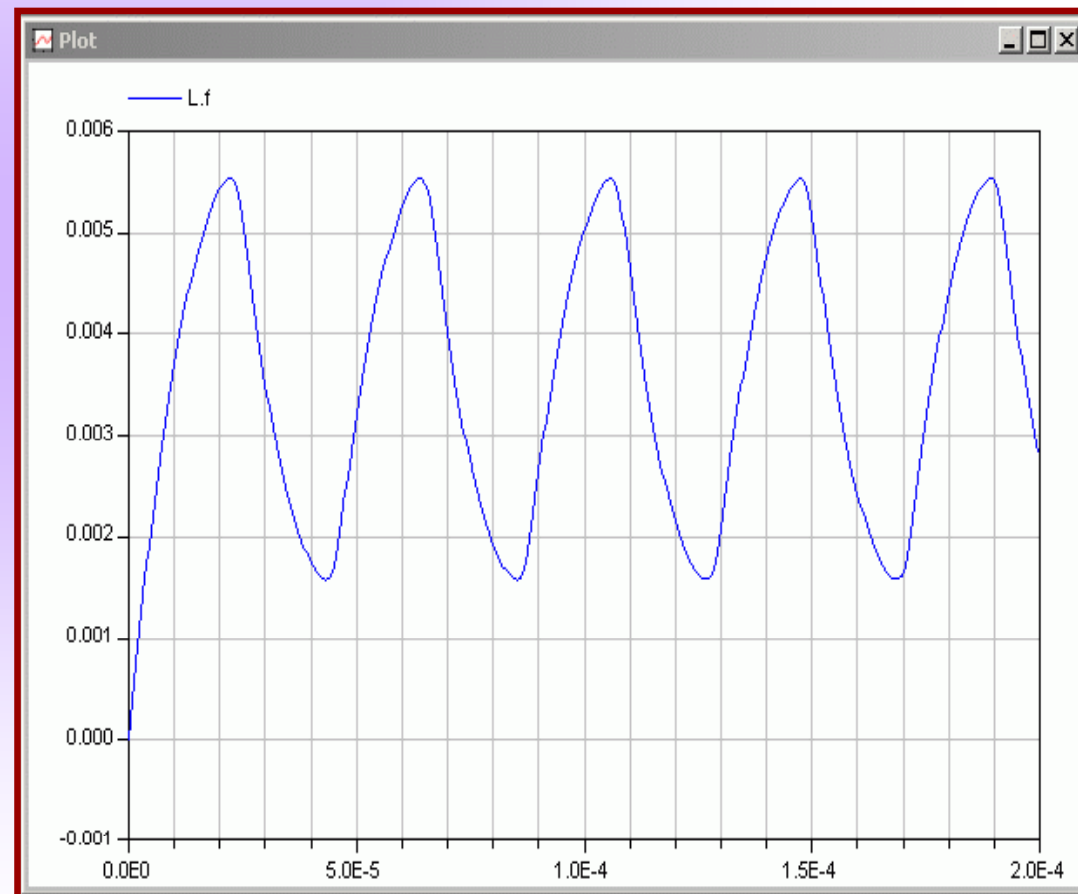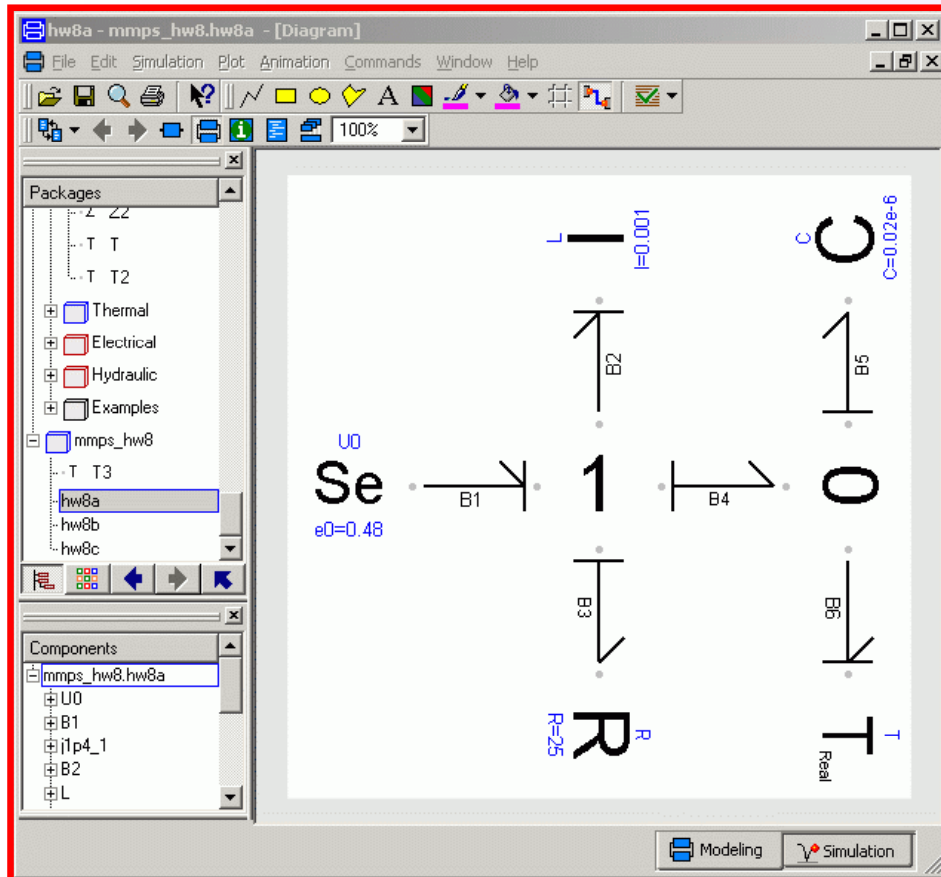- Now create a model of the overall circuit (without wrapping) in Dymola using the **BondLib** library as well as the previously coded **T3** model.
- Simulate the circuit across **0.2 msec** of simulated time.
- Plot the current through the tunnel diode.
- Interpret the results obtained.



Pulsed Tunnel Diode Circuit I


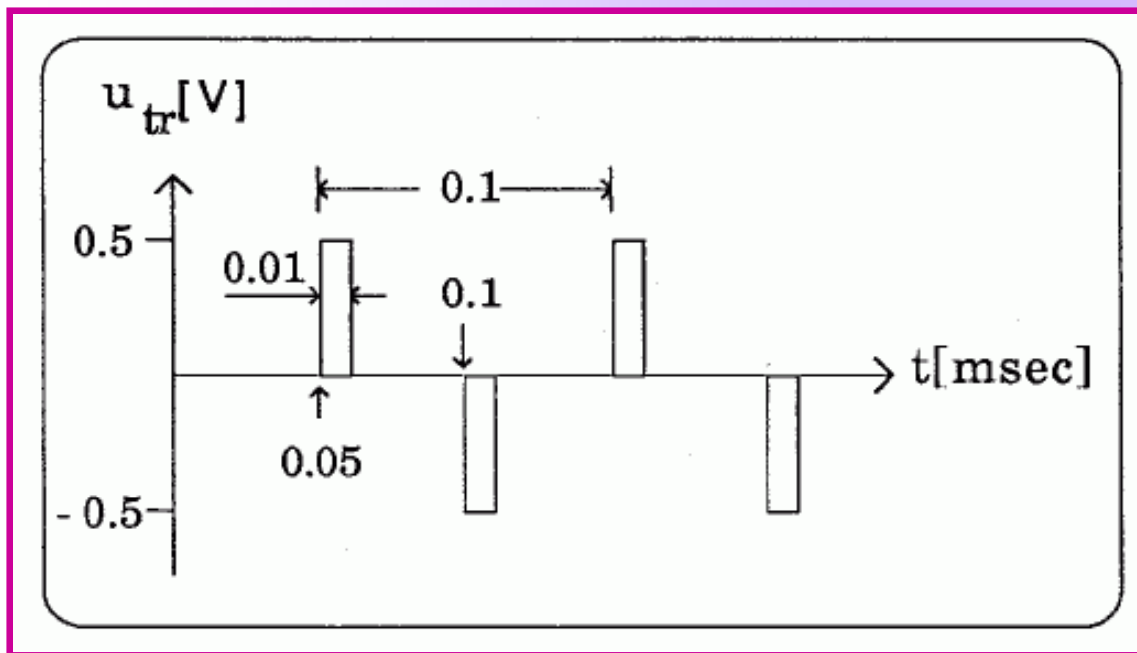
- In a second experiment, we include the following pulsed trigger signal, U_{tr} .



- You can easily create the trigger voltage out of the superposition of two of the pulsed voltage sources provided in the standard bond graph library.


Pulsed Tunnel Diode Circuit II

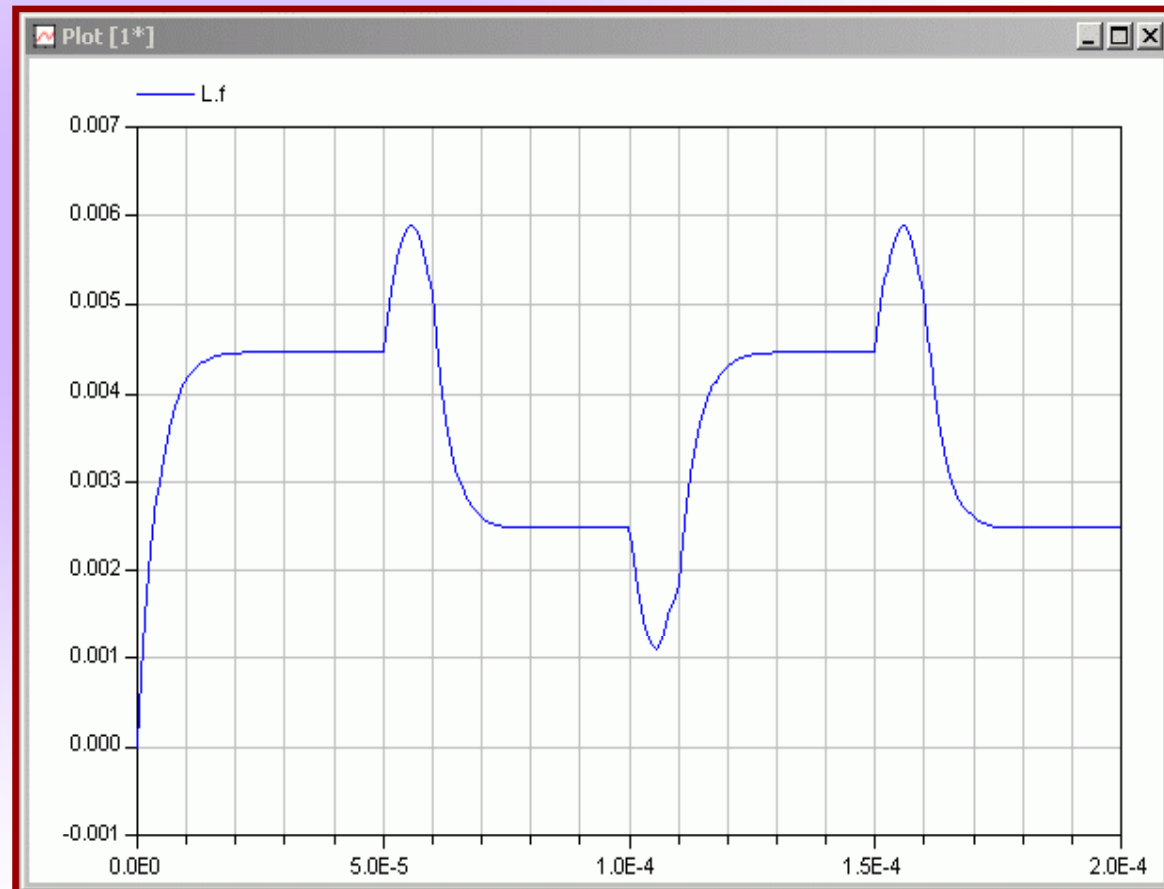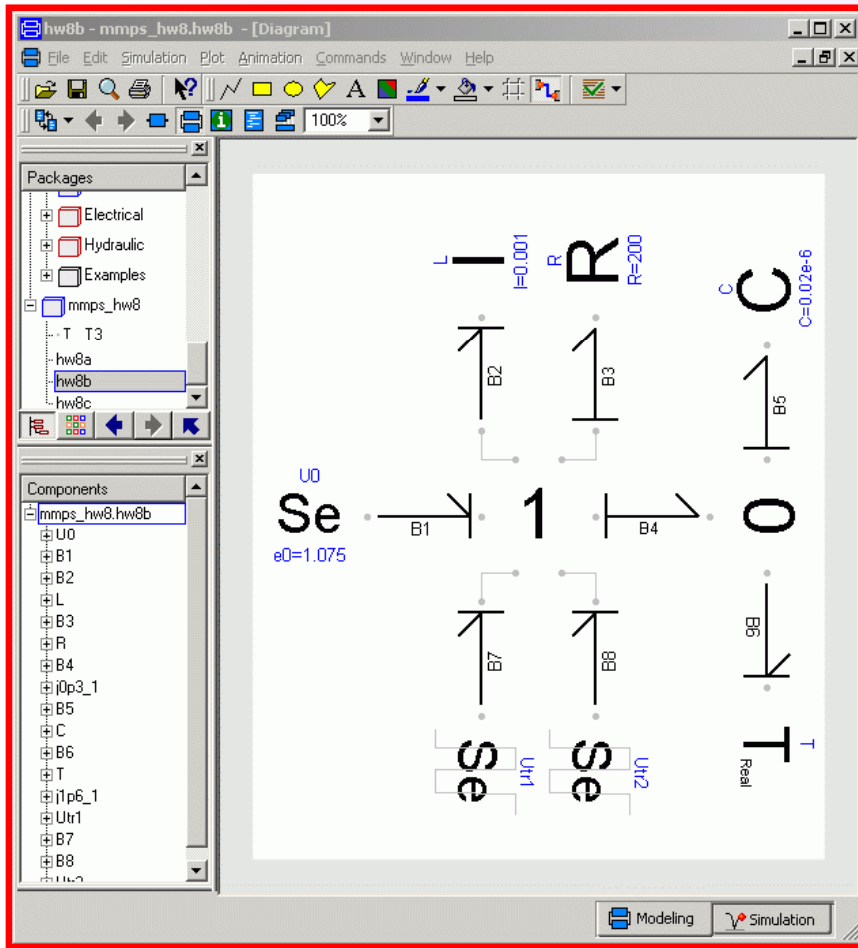- For this experiment, we select a resistor with a value of $R = 200 \, \Omega$. We now choose a DC bias of $U_0 = 1.075 \, V$.
- Simulate the modified circuit across $0.2 \, msec$ of simulated time.
- Plot the current through the tunnel diode.
- Interpret the results obtained.



Fly-back Power Converter Circuit I


- Given the electronic circuit:

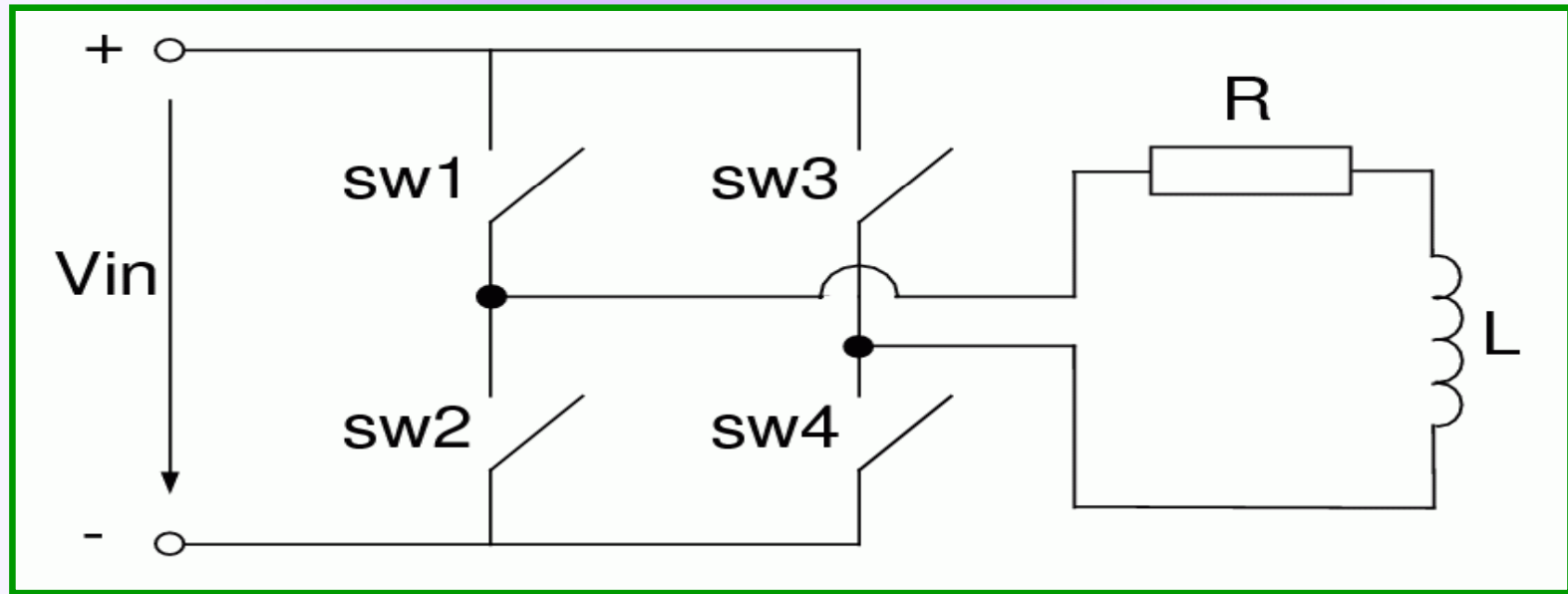

- The purpose is to create an inductor current that is approximately sinusoidal.

Fly-back Power Converter Circuit II

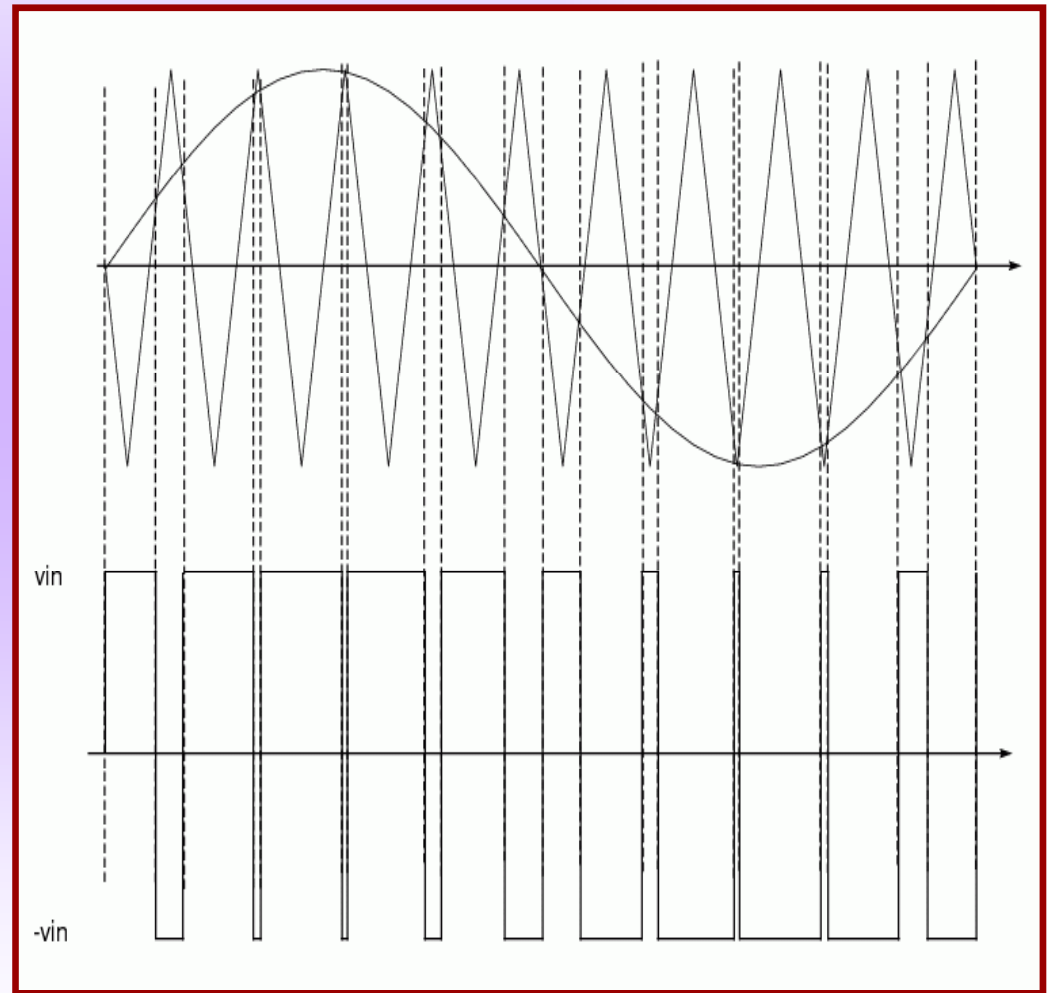- To this end, we use pulse width modulation.
- The four switches are controlled in such a way that sometimes V_{in} is being applied to the RL circuit, and at other times $-V_{in}$.
- The logic is explained in the graph to the right.



Fly-back Power Converter Circuit III


- If the sine-wave signal is larger than the triangular signal, switches #1 and #4 must be closed, whereas switches #2 and #3 must be opened.
- If the sine-wave signal is smaller than the triangular signal, switches #2 and #3 must be closed, whereas switches #1 and #4 must be opened.

Fly-back Power Converter Circuit IV

- We also want to implement a over-current protection circuit.
- When the inductor current becomes larger than **11.05 A**, switches #2 and #4 must be closed, and switches #1 and #3 must be opened, irrespective of what the previous logic indicated.
- When the inductor current becomes smaller than **10.95A**, the previous logic takes precedence once again.
- The hysteresis around the threshold current of **11.0 A** is necessary to avoid chattering.


Fly-back Power Converter Circuit V


- Without the hysteresis, the switches would switch back and forth with infinite frequency. This phenomenon is called chattering.
- Create a bond graph model of the fly-back converter circuit. Use causal bonds wherever the causality is fixed, and use a-causal bonds elsewhere.
- Make use of four “leaky” switches to avoid divisions by zero.
- Program the logic of the four switches graphically using the standard *Modelica* blocks library.

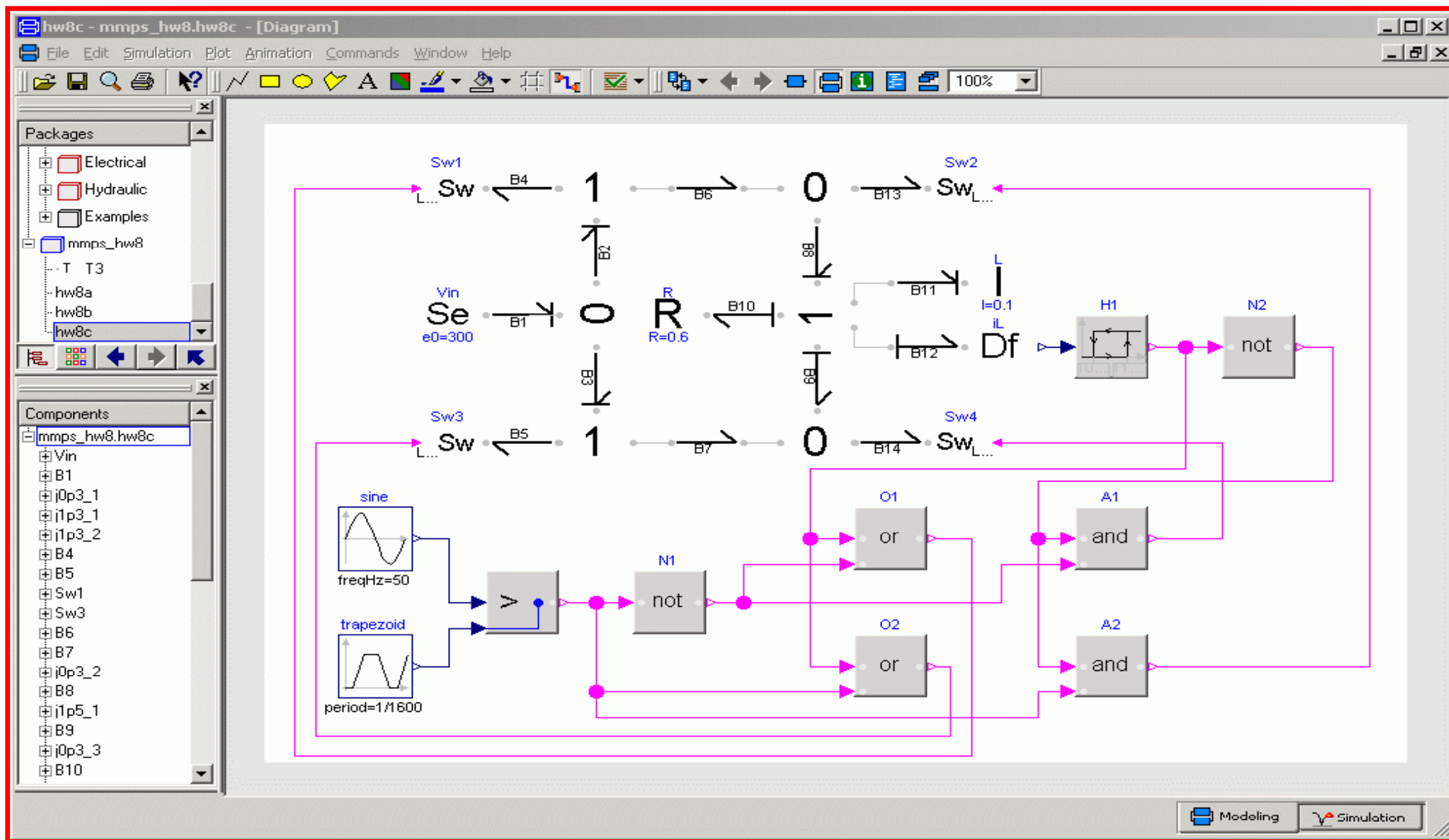


Fly-back Power Converter Circuit VI

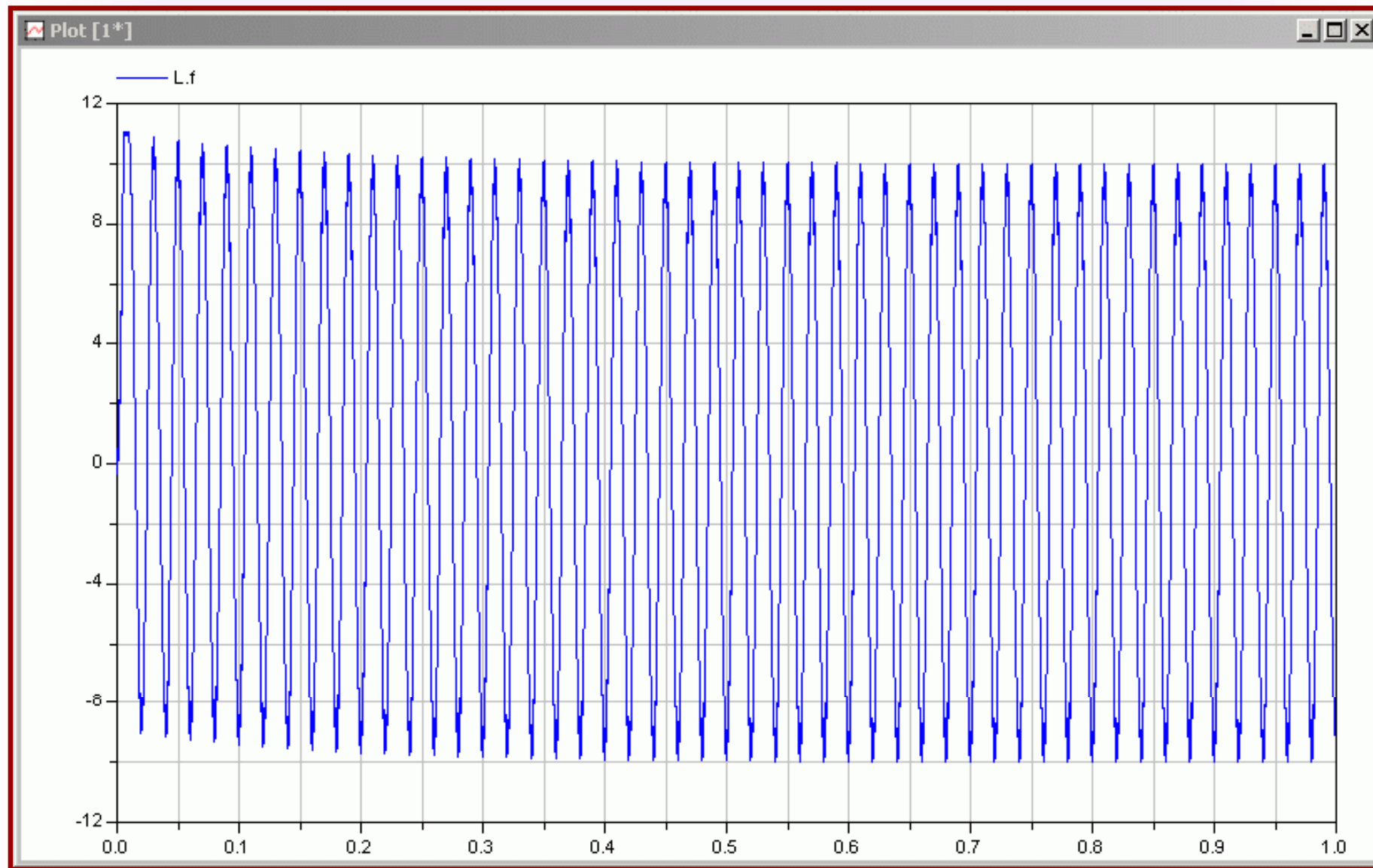- Simulate the circuit across *1 sec* of simulated time using $R = 0.6 \Omega$ and $L = 100 \text{ mH}$.
- Plot the inductor current over the entire period, and also over two smaller time windows, namely at an early period, when the over-current protection is active, and during steady-state operation.



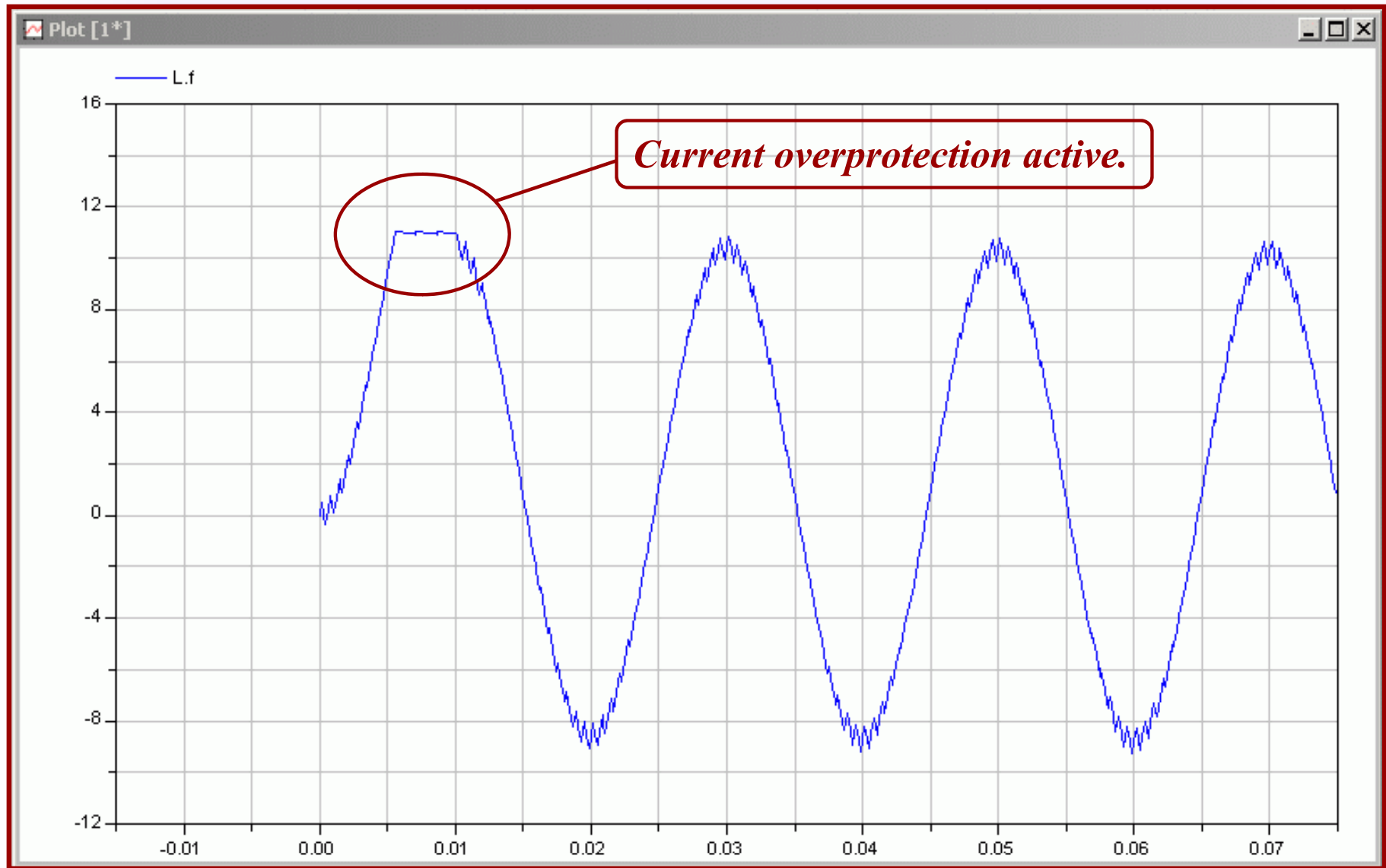

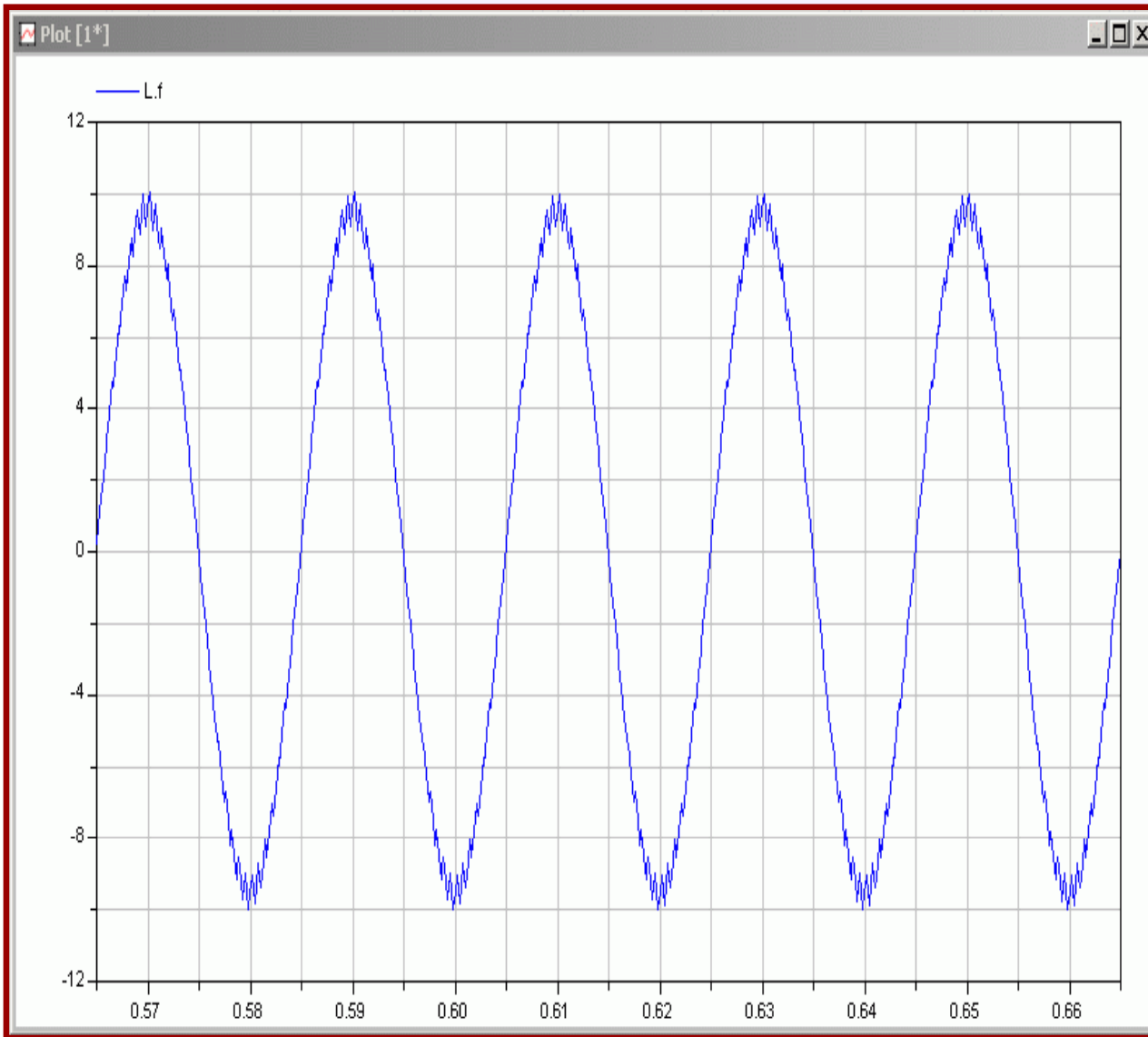

- The current is almost sinusoidal.
- There are only a few high-frequency components that could easily be filtered out using a low-pass filter.