

7th Homework – Solution

- In this homework, we shall model and simulate a discontinuous system as well as train the incorporation of tabular functions.
- We shall first model an electrical oscillatory circuit containing a tunnel diode.
- We shall then model a fly-back electronic power converter circuit with current overprotection.

November 8, 2012

© Prof. Dr. François E. Cellier

Start Presentation



- Free-running tunnel diode circuit
- Pulsed tunnel diode circuit
- Fly-back electronic power converter circuit

November 8, 2012


© Prof. Dr. François E. Cellier

Start Presentation



Free-running Tunnel Diode Circuit I

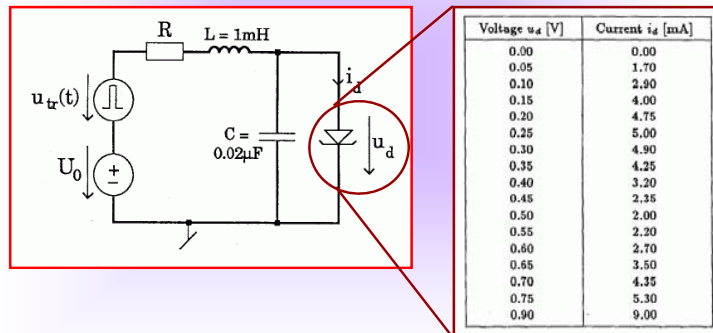- Given the following electronic circuit:



November 8, 2012

© Prof. Dr. François E. Cellier

Start Presentation



Free-running Tunnel Diode Circuit II

- Let us set $U_{tr} = 0$. We select a resistor with a value of $R = 25 \Omega$. We choose a DC bias of $U_0 = 0.48 V$.
- Create a bond graph (without wrapping) of the circuit. Use causal bonds whenever possible.
- Create a model **T3** representing the tunnel diode. The tabular function is incorporated by dragging the corresponding table-lookup block into the diagram window.
- Use Matlab to save the table onto a binary file, and reference that table from within the parameter window of the table-lookup block. Make sure to assign the correct causality to the table-lookup function. You can determine the correct causality from the bond graph of the overall circuit.

November 8, 2012


© Prof. Dr. François E. Cellier

Start Presentation



ETH
Eidgenössische Technische Hochschule Zürich
Swiss Federal Institute of Technology Zürich

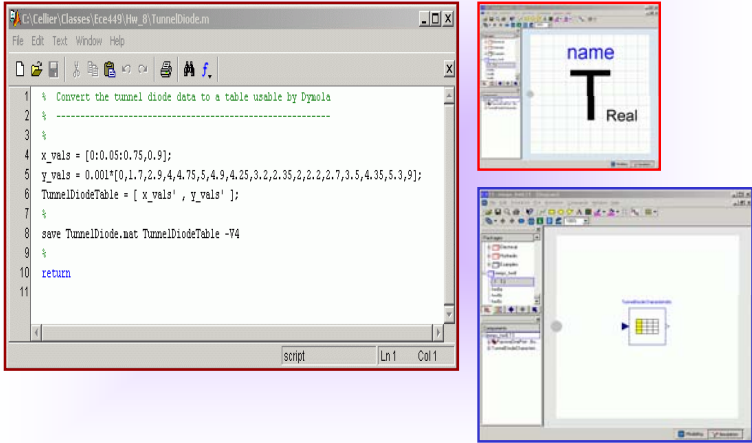Mathematical Modeling of Physical Systems




```

1 % Convert the tunnel diode data to a table usable by Dymola
2 %
3
4 x_vals = [0:0.05:0.75,0.9];
5
6 y_vals = 0.001*[0,1.7,2.9,4,4.75,5,4.9,4.25,3.2,2.35,2,2.2,2.7,3.5,4.35,5.3,9];
7
8 TunnelDiodeTable = [ x_vals' , y_vals' ];
9
10 save TunnelDiode.mat TunnelDiodeTable -v4
11
12 return
  
```

November 8, 2012 © Prof. Dr. François E. Cellier Start Presentation

ETH
Eidgenössische Technische Hochschule Zürich
Swiss Federal Institute of Technology Zürich

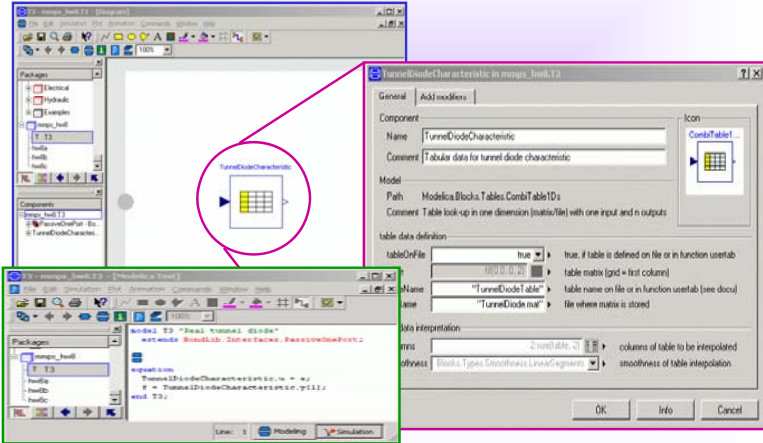Mathematical Modeling of Physical Systems



General | Add modifiers |
 Component:
 Name: TunnelDiodeCharacteristic
 Comment: Tabular data for tunnel diode characteristic
 Model:
 Path: Modelica.Blocks.Tables.CombineTables
 Comment: Table look-up in one dimension (matrix file) with one input and n outputs
 Table data definition:
 tableOnFile: true
 true, if table is defined on file or in function use tab
 tableMatrix: 10000 10000
 tableMatrix (grid = first column)
 Name: "TunnelDiodeTable"
 table name on file or in function use tab (see docu)
 fileWhereMatrixIsStored: "TunnelDiode.mat"
 file where matrix is stored
 Info interpretation:
 nns: 2 variables, 2
 columns of table to be interpolated
 smoothness: Blocks.Types.Smoothness.LinearSegments
 smoothness of table interpolation
 OK Info Cancel

November 8, 2012 © Prof. Dr. François E. Cellier Start Presentation

ETH
Eidgenössische Technische Hochschule Zürich
Swiss Federal Institute of Technology Zürich

Mathematical Modeling of Physical Systems


Free-running Tunnel Diode Circuit III

- Now create a model of the overall circuit (without wrapping) in Dymola using the **BondLib** library as well as the previously coded **T3** model.
- Simulate the circuit across **0.2 msec** of simulated time.
- Plot the current through the tunnel diode.
- Interpret the results obtained.


November 8, 2012 © Prof. Dr. François E. Cellier Start Presentation

ETH
Eidgenössische Technische Hochschule Zürich
Swiss Federal Institute of Technology Zürich

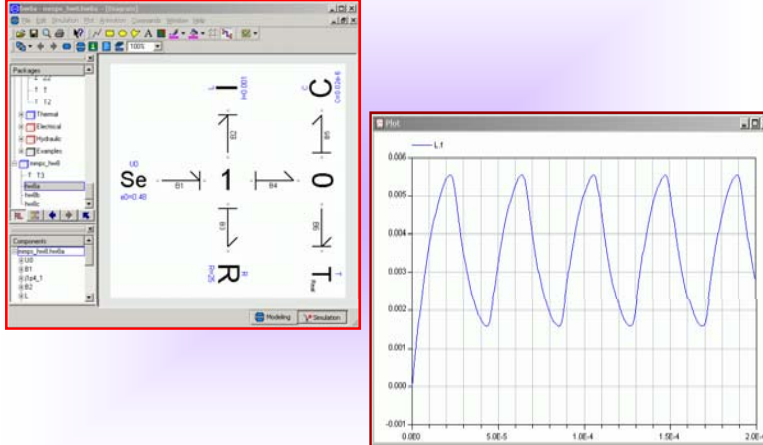Mathematical Modeling of Physical Systems



November 8, 2012 © Prof. Dr. François E. Cellier Start Presentation




Eidgenössische Technische Hochschule Zürich
Swiss Federal Institute of Technology Zurich


Mathematical Modeling of Physical Systems


Pulsed Tunnel Diode Circuit I

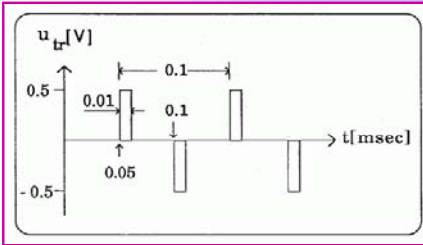- In a second experiment, we include the following pulsed trigger signal, U_{tr} .



- You can easily create the trigger voltage out of the superposition of two of the pulsed voltage sources provided in the standard bond graph library.

November 8, 2012
© Prof. Dr. François E. Cellier
Start Presentation 





Eidgenössische Technische Hochschule Zürich
Swiss Federal Institute of Technology Zurich

Mathematical Modeling of Physical Systems

Pulsed Tunnel Diode Circuit II

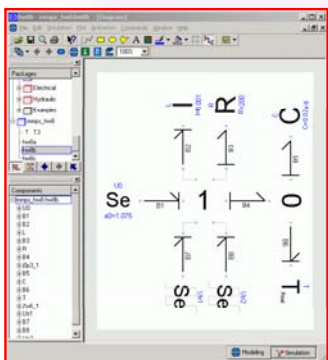

- For this experiment, we select a resistor with a value of $R = 200 \Omega$. We now choose a DC bias of $U_0 = 1.075 V$.
- Simulate the modified circuit across $0.2 msec$ of simulated time.
- Plot the current through the tunnel diode.
- Interpret the results obtained.


November 8, 2012
© Prof. Dr. François E. Cellier
Start Presentation 




Eidgenössische Technische Hochschule Zürich
Swiss Federal Institute of Technology Zurich

Mathematical Modeling of Physical Systems

November 8, 2012
© Prof. Dr. François E. Cellier
Start Presentation 




Eidgenössische Technische Hochschule Zürich
Swiss Federal Institute of Technology Zurich


Mathematical Modeling of Physical Systems


Fly-back Power Converter Circuit I

- Given the electronic circuit:

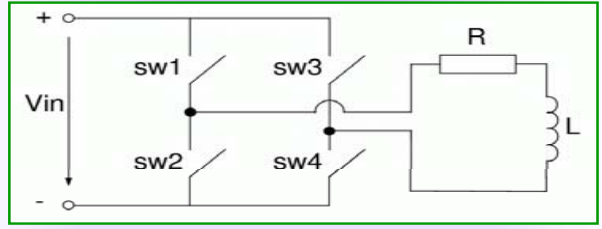

- The purpose is to create an inductor current that is approximately sinusoidal.

November 8, 2012
© Prof. Dr. François E. Cellier
Start Presentation 




Eidgenössische Technische Hochschule Zürich


Swiss Federal Institute of Technology Zürich


Mathematical Modeling of Physical Systems

Fly-back Power Converter Circuit II

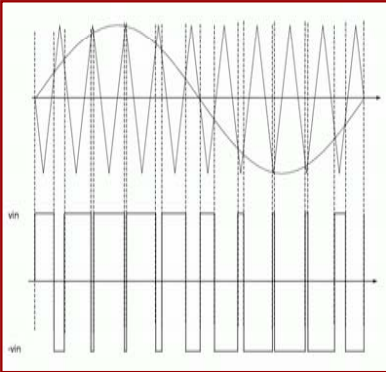- To this end, we use pulse width modulation.
- The four switches are controlled in such a way that sometimes V_{in} is being applied to the RL circuit, and at other times $-V_{in}$.
- The logic is explained in the graph to the right.



November 8, 2012
© Prof. Dr. François E. Cellier
Start Presentation





Eidgenössische Technische Hochschule Zürich


Swiss Federal Institute of Technology Zürich

Mathematical Modeling of Physical Systems

Fly-back Power Converter Circuit III

- If the sine-wave signal is larger than the triangular signal, switches #1 and #4 must be closed, whereas switches #2 and #3 must be opened.
- If the sine-wave signal is smaller than the triangular signal, switches #2 and #3 must be closed, whereas switches #1 and #4 must be opened.

November 8, 2012
© Prof. Dr. François E. Cellier
Start Presentation





Eidgenössische Technische Hochschule Zürich


Swiss Federal Institute of Technology Zürich

Mathematical Modeling of Physical Systems

Fly-back Power Converter Circuit IV

- We also want to implement a over-current protection circuit.
- When the inductor current becomes larger than 11.05 A , switches #2 and #4 must be closed, and switches #1 and #3 must be opened, irrespective of what the previous logic indicated.
- When the inductor current becomes smaller than 10.95 A , the previous logic takes precedence once again.
- The hysteresis around the threshold current of 11.0 A is necessary to avoid chattering.

November 8, 2012
© Prof. Dr. François E. Cellier
Start Presentation





Eidgenössische Technische Hochschule Zürich

Swiss Federal Institute of Technology Zürich

Mathematical Modeling of Physical Systems

Fly-back Power Converter Circuit V

- Without the hysteresis, the switches would switch back and forth with infinite frequency. This phenomenon is called chattering.
- Create a bond graph model of the fly-back converter circuit. Use causal bonds wherever the causality is fixed, and use a-causal bonds elsewhere.
- Make use of four “leaky” switches to avoid divisions by zero.
- Program the logic of the four switches graphically using the standard *Modelica* blocks library.

November 8, 2012
© Prof. Dr. François E. Cellier
Start Presentation


ETH
 Eidgenössische Technische Hochschule Zürich
 Swiss Federal Institute of Technology Zurich

Mathematical Modeling of Physical Systems

November 8, 2012

© Prof. Dr. François E. Cellier

Start Presentation

ETH
 Eidgenössische Technische Hochschule Zürich
 Swiss Federal Institute of Technology Zurich

Mathematical Modeling of Physical Systems

Fly-back Power Converter Circuit VI

- Simulate the circuit across **1 sec** of simulated time using $R = 0.6 \Omega$ and $L = 100 \text{ mH}$.
- Plot the inductor current over the entire period, and also over two smaller time windows, namely at an early period, when the over-current protection is active, and during steady-state operation.

November 8, 2012

© Prof. Dr. François E. Cellier

Start Presentation

ETH
 Eidgenössische Technische Hochschule Zürich
 Swiss Federal Institute of Technology Zurich

Mathematical Modeling of Physical Systems

November 8, 2012

© Prof. Dr. François E. Cellier

Start Presentation


ETH
 Eidgenössische Technische Hochschule Zürich
 Swiss Federal Institute of Technology Zurich

Mathematical Modeling of Physical Systems

November 8, 2012

© Prof. Dr. François E. Cellier

Start Presentation

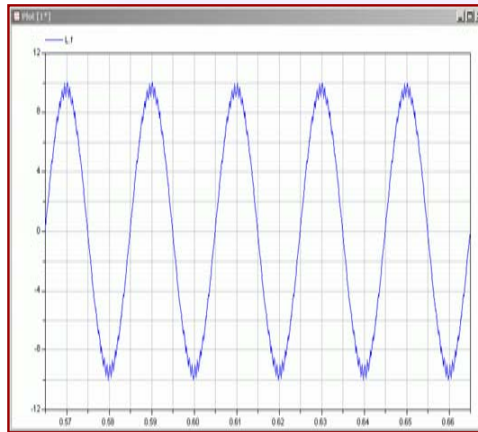

- The current is almost sinusoidal.
- There are only a few high-frequency components that could easily be filtered out using a low-pass filter.