

Electrical Circuits I

- This lecture discusses the mathematical modeling of simple electrical linear circuits.
- When modeling a circuit, one ends up with a set of implicitly formulated algebraic and differential equations (DAEs), which in the process of horizontal and vertical sorting are converted to a set of explicitly formulated algebraic and differential equations.
- By eliminating the algebraic variables, it is possible to convert these DAEs to a state-space representation.

September 20, 2012

© Prof. Dr. François E. Cellier

Start of Presentation 

Table of Contents

- Components and their models
- The circuit topology and its equations
- An example
- Horizontal sorting
- Vertical sorting
- State-space representation
- Transformation to state-space form


September 20, 2012

© Prof. Dr. François E. Cellier

Start of Presentation 

Linear Circuit Components


- Resistors

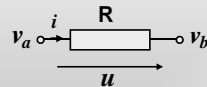

$$u = v_a - v_b$$


$$u = R \cdot i$$

- Capacitors

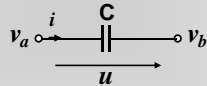

$$u = v_a - v_b$$
$$i = C \cdot \frac{du}{dt}$$

- Inductors

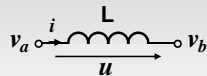

$$u = v_a - v_b$$

$$u = L \cdot \frac{di}{dt}$$


September 20, 2012

© Prof. Dr. François E. Cellier

Start of Presentation 

Linear Circuit Components II


- Voltage sources

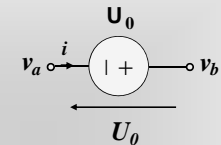

$$U_0 = v_b - v_a$$


$$U_0 = f(t)$$

- Current sources

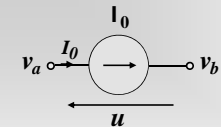

$$I_0 = f(t)$$

- Ground

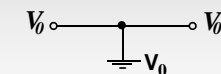


$$V_\theta = 0$$

September 20, 2012

© Prof. Dr. François E. Cellier

Start of Presentation 




Eidgenössische Technische Hochschule Zürich
 Swiss Federal Institute of Technology Zurich

Mathematical Modeling of Physical Systems


Circuit Topology

- Nodes

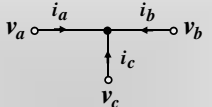


$v_a = v_b = v_c$
 $i_a + i_b + i_c = 0$

- Meshes

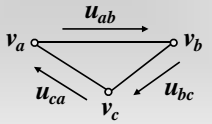

$u_{ab} + u_{bc} + u_{ca} = 0$


September 20, 2012
 © Prof. Dr. François E. Cellier
 Start of Presentation




Eidgenössische Technische Hochschule Zürich
 Swiss Federal Institute of Technology Zurich

Mathematical Modeling of Physical Systems

An Example I

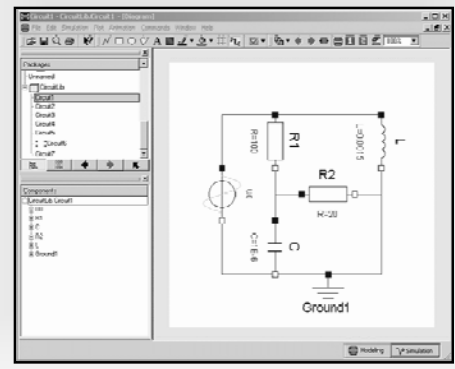

September 20, 2012
 © Prof. Dr. François E. Cellier
 Start of Presentation




Eidgenössische Technische Hochschule Zürich
 Swiss Federal Institute of Technology Zurich

Mathematical Modeling of Physical Systems

Rules for Systems of Equations I

- The component and topology equations contain a certain degree of redundancy.
- For example, it is possible to eliminate all potential variables (v_i) without problems.
- The current node equation for the ground node is redundant and is not used.
- The mesh equations are only used if the potential variables are being eliminated. If this is not the case, they are redundant.

September 20, 2012
 © Prof. Dr. François E. Cellier
 Start of Presentation




Eidgenössische Technische Hochschule Zürich
 Swiss Federal Institute of Technology Zurich

Mathematical Modeling of Physical Systems

Rules for Systems of Equations II

- If the potential variables are eliminated, every circuit component defines two variables: the current (i) through the element and the Voltage (u) across the element.
- Consequently, we need two equations to compute values for these two variables.
- One of the equations is the constituent equation of the element itself, the other comes from the topology.


September 20, 2012
 © Prof. Dr. François E. Cellier
 Start of Presentation



ETH
Eidgenössische Technische Hochschule Zürich
Swiss Federal Institute of Technology Zurich

Mathematical Modeling of Physical Systems

An Example II

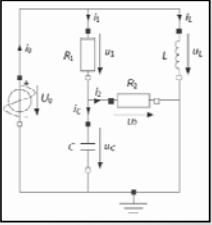

The circuit contains
5 components

⇒ We require 10
equations in 10
unknowns

Component equations:

$$U_0 = f(t) \quad i_C = C \cdot du_C/dt$$

$$u_1 = R_1 \cdot i_1 \quad u_L = L \cdot di_L/dt$$

$$u_2 = R_2 \cdot i_2$$

Node equations:


$$i_0 = i_1 + i_L \quad i_1 = i_2 + i_C$$

Mesh equations:

$$U_0 = u_1 + u_C \quad u_L = u_1 + u_2$$

$$u_C = u_2$$

September 20, 2012
© Prof. Dr. François E. Cellier
Start of Presentation ⇨



ETH
Eidgenössische Technische Hochschule Zürich
Swiss Federal Institute of Technology Zurich

Mathematical Modeling of Physical Systems

Rules for Horizontal Sorting I


- The time t may be assumed as known.
- The state variables (variables that appear in differentiated form) may be assumed as known.

$U_0 = f(t)$	$i_0 = i_1 + i_L$
$u_1 = R_1 \cdot i_1$	$i_1 = i_2 + i_C$
$u_2 = R_2 \cdot i_2$	$U_0 = u_1 + u_C$
$i_C = C \cdot du_C/dt$	$u_C = u_2$
$u_L = L \cdot di_L/dt$	$u_L = u_1 + u_2$

⇒

$U_0 = f(t)$	$i_0 = i_1 + i_L$
$u_1 = R_1 \cdot i_1$	$i_1 = i_2 + i_C$
$u_2 = R_2 \cdot i_2$	$U_0 = u_1 + u_C$
$i_C = C \cdot du_C/dt$	$u_C = u_2$
$u_L = L \cdot di_L/dt$	$u_L = u_1 + u_2$

September 20, 2012
© Prof. Dr. François E. Cellier
Start of Presentation ⇨



ETH
Eidgenössische Technische Hochschule Zürich
Swiss Federal Institute of Technology Zurich

Mathematical Modeling of Physical Systems

Rules for Horizontal Sorting II


- Equations that contain only one unknown must be solved for it.
- The solved variables are now known.

$U_0 = f(t)$	$i_0 = i_1 + i_L$
$u_1 = R_1 \cdot i_1$	$i_1 = i_2 + i_C$
$u_2 = R_2 \cdot i_2$	$U_0 = u_1 + u_C$
$i_C = C \cdot du_C/dt$	$u_C = u_2$
$u_L = L \cdot di_L/dt$	$u_L = u_1 + u_2$

⇒

$U_0 = f(t)$	$i_0 = i_1 + i_L$
$u_1 = R_1 \cdot i_1$	$i_1 = i_2 + i_C$
$u_2 = R_2 \cdot i_2$	$U_0 = u_1 + u_C$
$i_C = C \cdot du_C/dt$	$u_C = u_2$
$u_L = L \cdot di_L/dt$	$u_L = u_1 + u_2$

September 20, 2012
© Prof. Dr. François E. Cellier
Start of Presentation ⇨



ETH
Eidgenössische Technische Hochschule Zürich
Swiss Federal Institute of Technology Zurich

Mathematical Modeling of Physical Systems

Rules for Horizontal Sorting III

- Variables that show up in only one equation must be solved for using that equation.

$U_0 = f(t)$	$i_0 = i_1 + i_L$
$u_1 = R_1 \cdot i_1$	$i_1 = i_2 + i_C$
$u_2 = R_2 \cdot i_2$	$U_0 = u_1 + u_C$
$i_C = C \cdot du_C/dt$	$u_C = u_2$
$u_L = L \cdot di_L/dt$	$u_L = u_1 + u_2$

⇒

$U_0 = f(t)$	$i_0 = i_1 + i_L$
$u_1 = R_1 \cdot i_1$	$i_1 = i_2 + i_C$
$u_2 = R_2 \cdot i_2$	$U_0 = u_1 + u_C$
$i_C = C \cdot du_C/dt$	$u_C = u_2$
$u_L = L \cdot di_L/dt$	$u_L = u_1 + u_2$

September 20, 2012
© Prof. Dr. François E. Cellier
Start of Presentation ⇨

Rules for Horizontal Sorting IV

- All rules may be used recursively.

$U_0 = f(t)$
$u_1 = R_1 \cdot i_1$
$u_2 = R_2 \cdot i_2$
$i_C = C \cdot du_C/dt$
$u_L = L \cdot di_L/dt$

\Rightarrow

$U_0 = f(t)$
$u_1 = R_1 \cdot i_1$
$u_2 = R_2 \cdot i_2$
$i_C = C \cdot du_C/dt$
$u_L = L \cdot di_L/dt$

September 20, 2012

© Prof. Dr. François E. Cellier

Start of Presentation 

Mathematical Modeling of Physical Systems

The algorithm is applied, until every equation defines exactly one variable that is being solved for.

$U_0 = f(t)$	$i_0 = i_1 + i_L$
$u_1 = R_1 \cdot i_1$	$i_1 = i_2 + i_C$
$u_2 = R_2 \cdot i_2$	$U_0 = u_1 + u_C$
$i_C = C \cdot du_C/dt$	$u_C = u_2$
$u_L = L \cdot di_L/dt$	$u_L = u_1 + u_2$

\Rightarrow

$U_0 = f(t)$	$i_0 = i_1 + i_L$
$u_1 = R_1 \cdot i_1$	$i_1 = i_2 + i_C$
$u_2 = R_2 \cdot i_2$	$U_0 = u_1 + u_C$
$i_C = C \cdot du_C/dt$	$u_C = u_2$
$u_L = L \cdot di_L/dt$	$u_L = u_1 + u_2$

\Downarrow

$U_0 = f(t)$	$i_0 = i_1 + i_L$
$u_1 = R_1 \cdot i_1$	$i_1 = i_2 + i_C$
$u_2 = R_2 \cdot i_2$	$U_0 = u_1 + u_C$
$i_C = C \cdot du_C/dt$	$u_C = u_2$
$u_L = L \cdot di_L/dt$	$u_L = u_1 + u_2$

September 20, 2012

© Prof. Dr. François E. Cellier

Start of Presentation 

Mathematical Modeling of Physical Systems

Rules for Horizontal Sorting V

- The horizontal sorting can now be performed using symbolic formula manipulation techniques.

$U_0 = f(t)$
$u_1 = R_1 \cdot i_1$
$u_2 = R_2 \cdot i_2$
$i_C = C \cdot du_C/dt$
$u_L = L \cdot di_L/dt$

\Rightarrow

$U_0 = f(t)$
$i_1 = u_1 / R_1$
$i_2 = u_2 / R_2$
$du_C/dt = i_C / C$
$di_L/dt = u_L / L$

$i_0 = i_1 + i_L$
$i_1 = i_2 + i_C$
$U_0 = u_1 + u_C$
$u_C = u_2$
$u_L = u_1 + u_2$

$i_0 = i_1 + i_L$
$i_C = i_1 - i_2$
$u_1 = U_0 - u_C$
$u_2 = u_C$
$u_L = u_1 + u_2$

September 20, 2012

© Prof. Dr. François E. Cellier

Start of Presentation 

Mathematical Modeling of Physical Systems

Rules for Vertical Sorting

- By now, the equations have become assignment statements. They can be sorted vertically, such that no variable is being used before it has been defined.

$U_0 = f(t)$
$i_1 = u_1/R_1$
$i_2 = u_2/R_2$
$du_C/dt = i_C/C$
$di_L/dt = u_L/L$

\Rightarrow

$U_0 = f(t)$
$u_1 = U_0 - u_C$
$i_1 = u_1/R_1$
$i_0 = i_1 + i_L$
$u_2 = u_C$

$i_2 = u_2/R_2$
$i_C = i_1 - i_2$
$u_L = u_1 + u_2$
$du_C/dt = i_C/C$
$di_L/dt = u_L/L$

September 20, 2012

© Prof. Dr. François E. Cellier

Start of Presentation 

Conversion to State-space Form I

$U_0 - f(t)$	$i_2 = u_2/R_2$
$u_1 = U_0 - u_C$	$i_C = i_1 - i_2$
$i_1 = u_1/R_1$	$u_L = u_1 + u_2$
$i_0 = i_1 + i_L$	$du_C/dt = i_C/C$
$u_2 = u_C$	$di_L/dt = u_L/L$

$$\Rightarrow$$

$$\begin{aligned}
 du_C/dt &= i_C/C \\
 &= (i_1 - i_2)/C \\
 &= i_1/C - i_2/C \\
 &= u_1/(R_1 \cdot C) - u_2/(R_2 \cdot C) \\
 &= (U_0 - u_C)/(R_1 \cdot C) - u_C/(R_2 \cdot C) \\
 di_L/dt &= u_L/L \\
 &= (u_1 + u_2)/L \\
 &= u_1/L + u_2/L \\
 &= (U_0 - u_C)/L + u_C/L \\
 &= U_0/L
 \end{aligned}$$

September 20, 2012

© Prof. Dr. François E. Cellier

Start of Presentation 

Conversion to State-space Form II

We let:


$$\left\{ \begin{array}{l} x_1 = u_C \\ x_2 = i_L \\ u = U_\theta \\ y = u_C \end{array} \right. \Rightarrow \left\{ \begin{array}{l} \dot{x}_1 = - \left[\frac{1}{R_1 \cdot C} + \frac{1}{R_2 \cdot C} \right] x_1 + \frac{1}{R_1 \cdot C} \cdot u \\ \dot{x}_2 = \frac{1}{L} \cdot u \\ y = x_1 \end{array} \right.$$

September 20, 2012

© Prof. Dr. François E. Cellier

Start of Presentation 

An Example IV

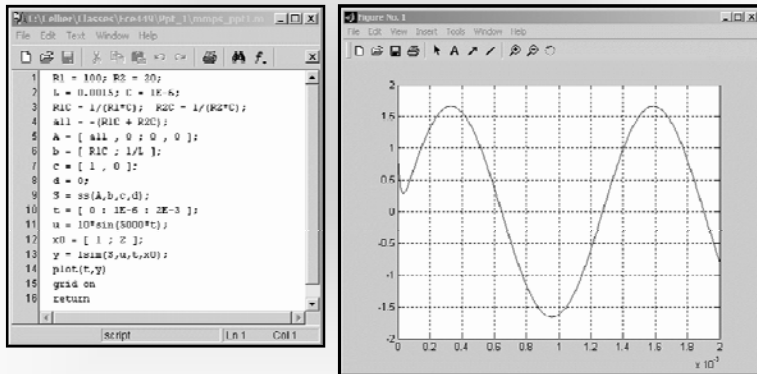

September 20, 2012

© Prof. Dr. François E. Cellier

Start of Presentation 

References

- Cellier, F.E. (1991), Continuous System Modeling, Springer-Verlag, New York, Chapter 3.
- Cellier, F.E. (2001), Matlab code of circuit example.

September 20, 2012

© Prof. Dr. François E. Cellier

Start of Presentation 