



Einige eine Stehn ische Hochschule Zühlch Swiss-Federal Institute al Technology Zuhlch	Mathematical Modeling	of Physical Systems
Algebraic	Loops: An Exa	mple
+a +a	Component equations:	
	$U_0 = f(t)$	$u_3 = R_3 \cdot i_3$
	$u_1 = R_1 \cdot i_1$	$u_L = L \cdot di_L/dt$
	$u_2 = R_2 \cdot i_2$	
R3 us	Node equations:	
	$i_0 = i_I + i_L$	$i_1 = i_2 + i_3$
The circuit contains 5 components	Mesh equations:	
⇒ We require	$U_0 = u_1 + u_3$	$u_L = u_1 + u_2$
10 equations in 10 unknowns	$u_3 = u_2$	
September 27, 2012 © Pro	of. Dr. François E. Cellier	Start of presentation

	warshe restanciale Webback with a second sec					
	Horizontal Sorting I					
1.	$U_0 = f(t)$	$i_0 = i_I + i_L$	2.	$U_0 = f(t)$	$i_0 = i_I + i_L$	
	$u_1 = R_1 \cdot i_1$	$i_1 = i_2 + i_3$		$u_I = R_I \cdot i_I$	$i_1 = i_2 + i_3$	
	$u_2 = R_2 \cdot i_2$	$U_0 = u_1 + u_3$		$u_2 = R_2 \cdot i_2$	$U_0 = u_1 + u_3$	
	$u_3 = R_3 \cdot i_3$	$u_3 = u_2$		$u_3 = R_3 \cdot i_3$	$u_3 = u_2$	
	$u_L = L \cdot di_L/dt$	$u_L = u_1 + u_2$		$u_L = L \cdot di_L/dt$	$u_L = u_1 + u_2$	
3.	$U_0 = f(t)$	$i_0 = i_1 + i_L$	4.	$U_0 = f(t)$	$i_0 = i_I + i_L$	
	$u_I = \boldsymbol{R}_I \cdot \boldsymbol{i}_I$	$i_1 = i_2 + i_3$		$u_I = R_I \cdot i_I$	$i_1 = i_2 + i_3$	
	$u_2 = R_2 \cdot i_2$	$\boldsymbol{U_0} = \boldsymbol{u_1} + \boldsymbol{u_3}$		$u_2 = R_2 \cdot i_2$	$\boldsymbol{U_0} = \boldsymbol{u_1} + \boldsymbol{u_3}$	
	$u_3 = R_3 \cdot i_3$	$u_3 = u_2$		$u_3 = R_3 \cdot i_3$	$u_3 = u_2$	
	$u_L = L \cdot di_L/dt$	$u_L = u_1 + u_2$		$u_L = L \cdot di_L/dt$	$u_L = u_1 + u_2$	
Septemb	September 27, 2012 © Prof. Dr. François E. Cellier Start of presentation					









































